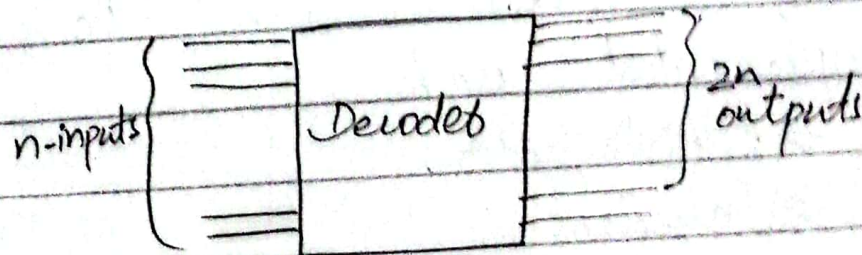


(Unit #6)

Decoders:-

Definition:-

Decoder is a combinational logic circuit with multi-input and multiple-output which decodes n inputs into 2^n possible outputs.



where E : Enable $\rightarrow E: 0$ Decoder is disabled.
 $\rightarrow E: 1$ Decoder is enabled

The basic binary function:

$\rightarrow$ An AND gate can be used as the basic decoding element because it produces a High output only when all inputs are High.

Decoded connect coded information into familiar or non coded form.

→ If an active-High output is required for each decoded number, the entire decoder can be implemented with

- AND gates
- Inverters

If an active low output is required for each decoded number, the entire decoder can be implemented with

- NAND gates
- Inverters

Types of Decoder

Types of decoder are as follows:

- 2 to 4 Binary Decoder
- 3 to 8 Binary Decoder
- BCD to decimal Decoder
- BCD to Seven Segment Decoder


2⁴ = 8

0x1⁴

2-to-4 Binary Decoder

Truth table:-

Dec	A ₀	A ₁	High				Low			
			D ₀	D ₁	D ₂	D ₃	D ₀	D ₁	D ₂	D ₃
0	0	0	1	0	0	0	0	1	1	1
1	0	1	0	1	0	0	1	0	1	1
2	1	0	0	0	1	0	1	1	0	1
3	1	1	0	0	0	1	1	1	1	0

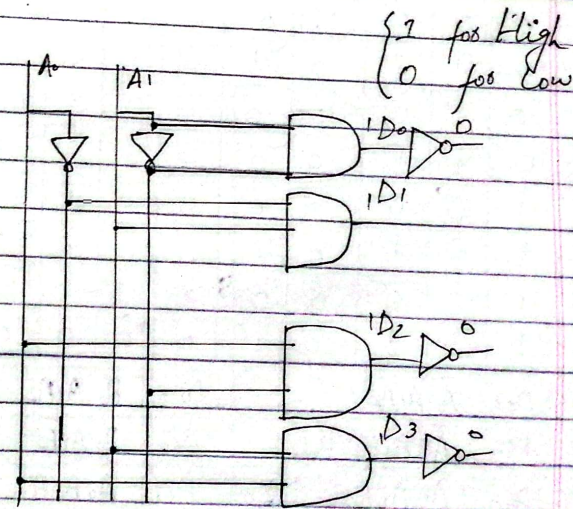

$$D_0 = \bar{A}_0 \bar{A}_1 \quad D_2 = A_0 \bar{A}_1$$

$$D_1 = \bar{A}_0 A_1 \quad D_3 = A_0 A_1$$

A ₀	Decodes 2x4	D ₀
A ₁		D ₁
		D ₂
		D ₃

3-to-8 Binary Decoder

Truth table:

High

Decimal	A ₀	A ₁	A ₂	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	0	0	0	0
2	0	1	0	0	0	1	0	0	0	0	0
3	0	1	1	0	0	0	1	0	0	0	0
4	1	0	0	0	0	0	0	1	0	0	0
5	1	0	1	0	0	0	0	0	1	0	0
6	1	1	0	0	0	0	0	0	0	1	0
7	1	1	1	0	0	0	0	0	0	0	1

$$D_0 = \bar{A}_0 \bar{A}_1 \bar{A}_2$$

$$D_1 = \bar{A}_0 \bar{A}_1 A_2$$

$$D_2 = \bar{A}_0 A_1 \bar{A}_2$$

$$D_3 = \bar{A}_0 A_1 A_2$$

$$D_4 = A_0 \bar{A}_1 \bar{A}_2$$

$$D_5 = A_0 \bar{A}_1 A_2$$


$$D_6 = A_0 A_1 \bar{A}_2$$

$$D_7 = A_0 A_1 A_2$$

$$D_8 =$$

Low


D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	1	1	1	1	1	1	1
1	0	1	1	1	1	1	1
1	1	0	1	1	1	1	1
1	1	1	0	1	1	1	1
1	1	1	1	0	1	1	1
1	1	1	1	1	0	1	1
1	1	1	1	1	1	0	1
1	1	1	1	1	1	1	0

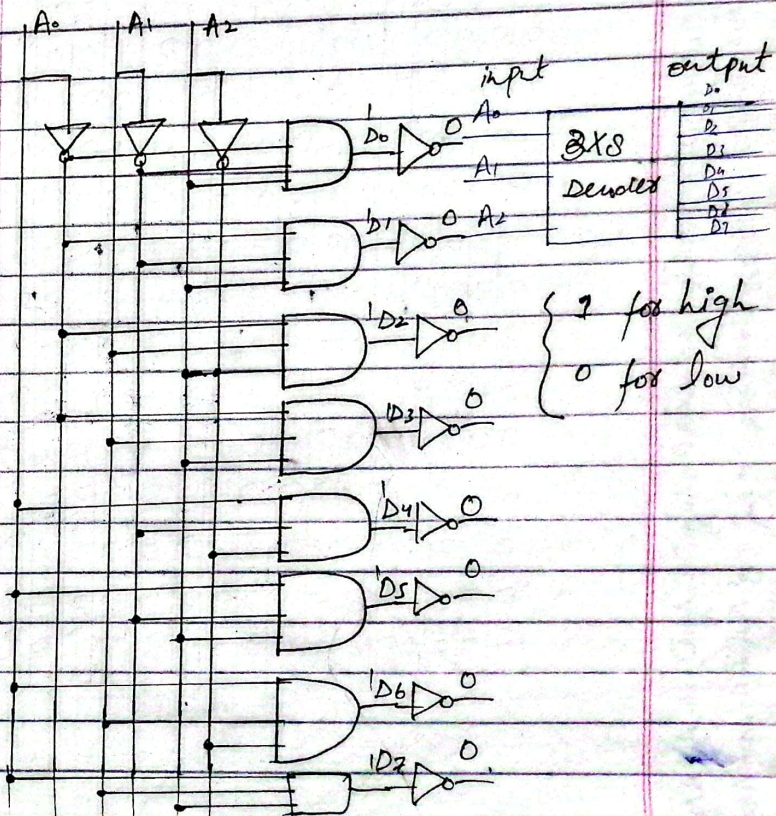


4-to-16 Decoder:-

$D_0 = \bar{A}_0 \bar{A}_1 \bar{A}_2 \bar{A}_3$, $D_1 = \bar{A}_0 \bar{A}_1 \bar{A}_2 A_3$, $D_2 = \bar{A}_0 \bar{A}_1 A_2 \bar{A}_3$, $D_3 = \bar{A}_0 \bar{A}_1 A_2 A_3$, $D_4 = \bar{A}_0 A_1 \bar{A}_2 \bar{A}_3$, $D_5 = \bar{A}_0 A_1 \bar{A}_2 A_3$, $D_6 = \bar{A}_0 A_1 A_2 \bar{A}_3$, $D_7 = \bar{A}_0 A_1 A_2 A_3$, $D_8 = A_0 \bar{A}_1 \bar{A}_2 \bar{A}_3$, $D_9 = A_0 \bar{A}_1 \bar{A}_2 A_3$, $D_{10} = A_0 \bar{A}_1 A_2 \bar{A}_3$, $D_{11} = A_0 \bar{A}_1 A_2 A_3$, $D_{12} = A_0 A_1 \bar{A}_2 \bar{A}_3$, $D_{13} = A_0 A_1 \bar{A}_2 A_3$, $D_{14} = A_0 A_1 A_2 \bar{A}_3$, $D_{15} = A_0 A_1 A_2 A_3$

	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
2	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
3	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
4	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
5	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
6	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
7	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
8	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
9	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
10	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
11	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
12	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
13	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
14	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
15	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

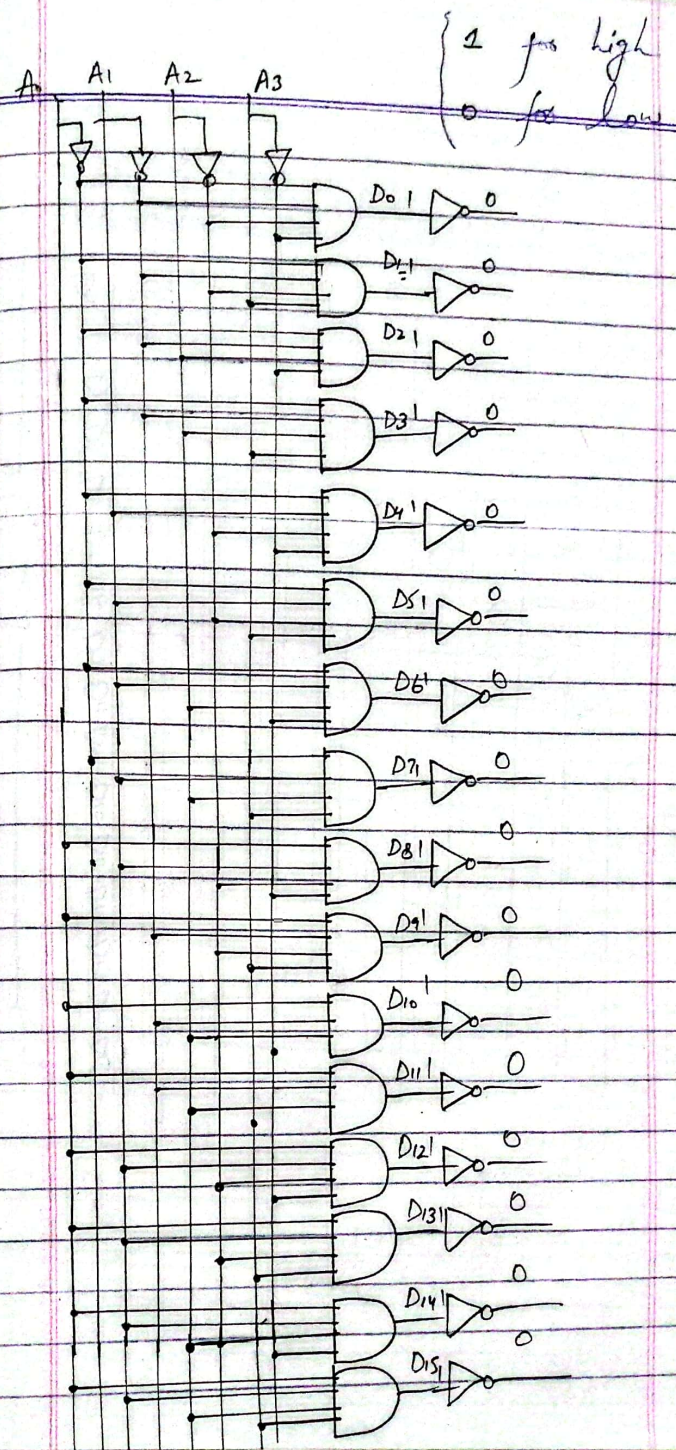


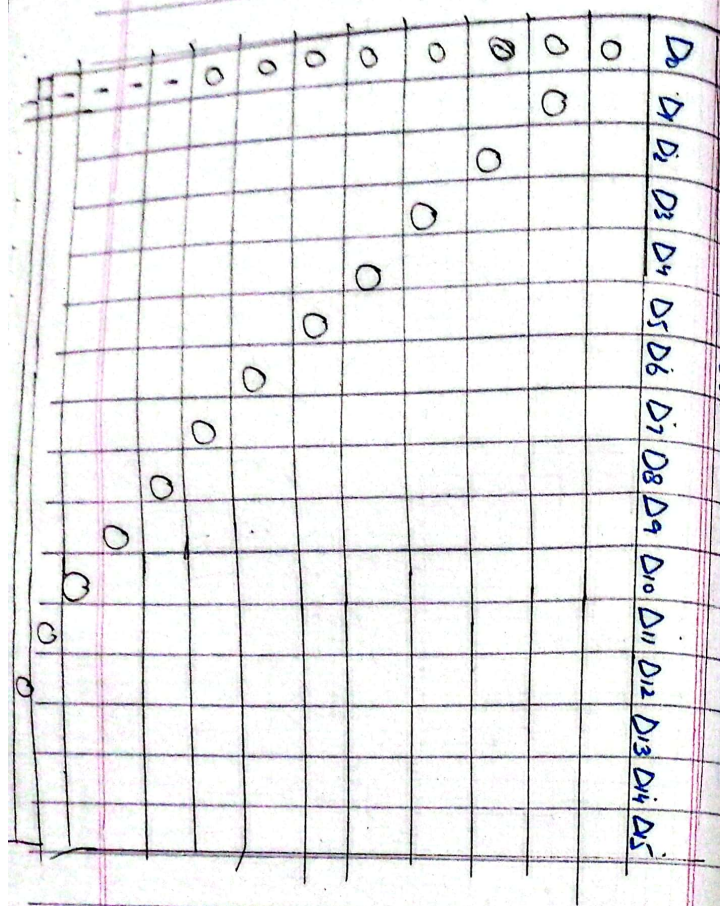


BCD to Decimal Decoder

4x10 decoder

	A	B	C	D										
D	A ₀	A ₁	A ₂	A ₃	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	D ₈	D ₉
0	0	0	0	0	1	0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	1	0	0	0	0	0	0	0	0
2	0	0	1	0	0	0	1	0	0	0	0	0	0	0
3	0	0	1	1	0	0	0	1	0	0	0	0	0	0
4	0	1	0	0	0	0	0	0	1	0	0	0	0	0
5	0	1	0	1	0	0	0	0	0	1	0	0	0	0
6	0	1	1	0	0	0	0	0	0	0	1	0	0	0
7	0	1	1	1	0	0	0	0	0	0	0	1	0	0
8	1	0	0	0	0	0	0	0	0	0	0	0	1	0
9	1	0	0	1	0	0	0	0	0	0	0	0	0	1

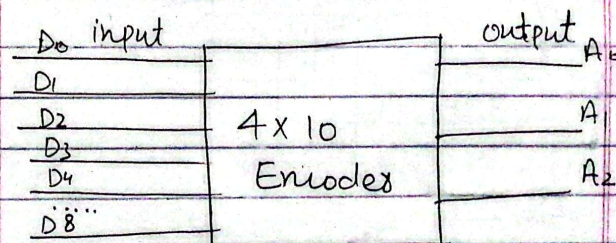


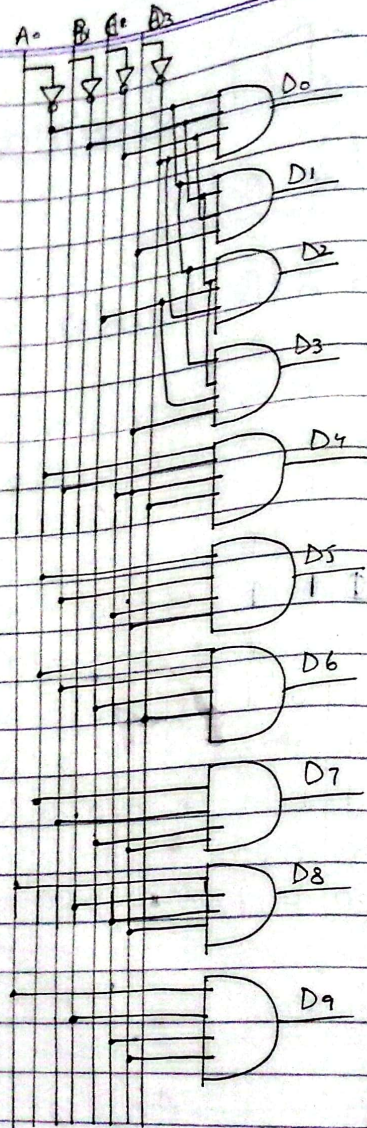$D_0 = \bar{A}\bar{B}\bar{C}\bar{D}$
 $D_1 = \bar{A}\bar{B}\bar{C}D$
 $D_2 = \bar{A}\bar{B}C\bar{D}$
 $D_3 = \bar{A}\bar{B}CD$
 $D_4 = \bar{A}B\bar{C}\bar{D}$
 $D_5 = \bar{A}B\bar{C}D$
 $D_6 = \bar{A}BC\bar{D}$
 $D_7 = \bar{A}BCD$
 $D_8 = A\bar{B}\bar{C}\bar{D}$
 $D_9 = A\bar{B}\bar{C}D$



Encoders:-

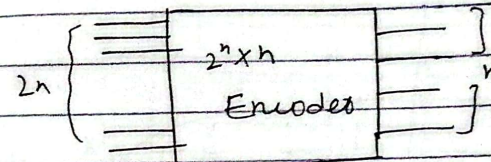→ Encoder is a logic circuit which performs the opposite action of the decoder.
 → 2^n i/p lines and n o/p lines



→ Encoder converts binary information in the form of a 2^n i/p lines into n o/p lines, which represent 'n' code for the i/p.

Example


		Input				Output	
		D_3	D_2	D_1	D_0	X	Y
D_0	X	0	0	0	1	0	0
D_1	X	0	0	1	0	0	1
D_2		0	1	0	0	1	0
D_3		1	0	0	0	1	1

Implementation:-

$$X = D_2 + D_3$$

$$Y = D_1 + D_3$$

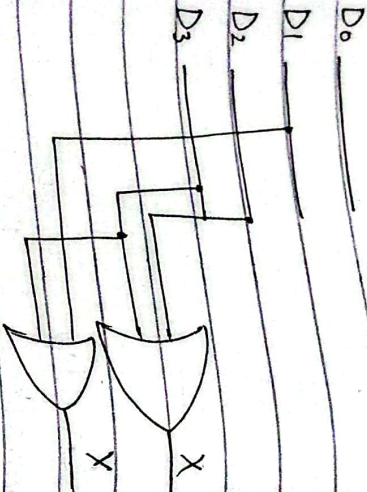→ Encoder can be realised with 'OR' gates.




Implementation:-

$$A_0 = D_4 + D_5 + D_6 + D_7$$


$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_1 + D_3 + D_5 + D_7$$

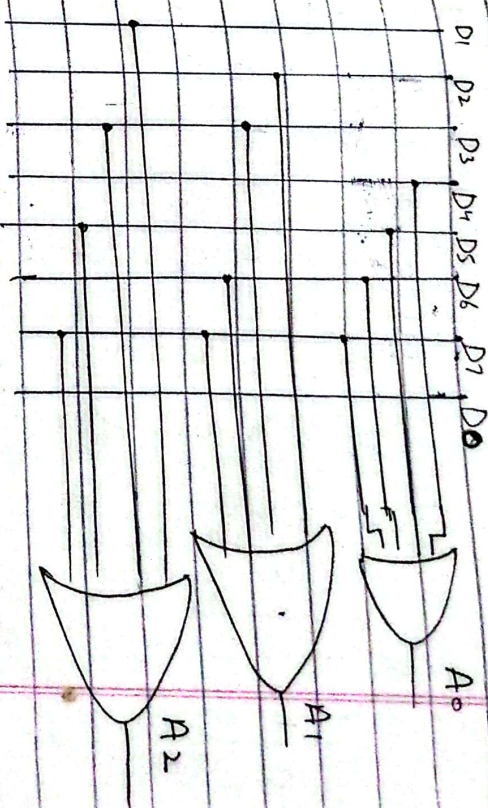

Decimal to BCD Encoder:-

10 X 4

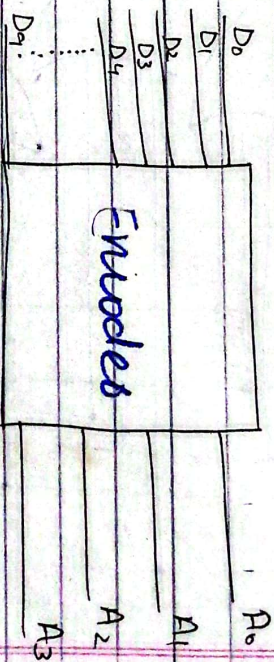

8x3 Encoder:-

D7	D6	D5	D4	D3	D2	D1	D0	A2	A1	A0
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	1	0	0	0	0	0	0
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0

input										output	
D ₉	D ₈	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₃	A ₂
0	0	0	0	0	0	0	0	0	1	0	0
0	0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	1	0	0	0	0	0
0	0	0	0	0	1	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	1	0	0


Implementation:-

$$A_0 = D_0 + D_2 + D_4 + D_6 + D_8$$

$$A_1 = D_1 + D_3 + D_5 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

$$A_3 = D_8 + D_9$$

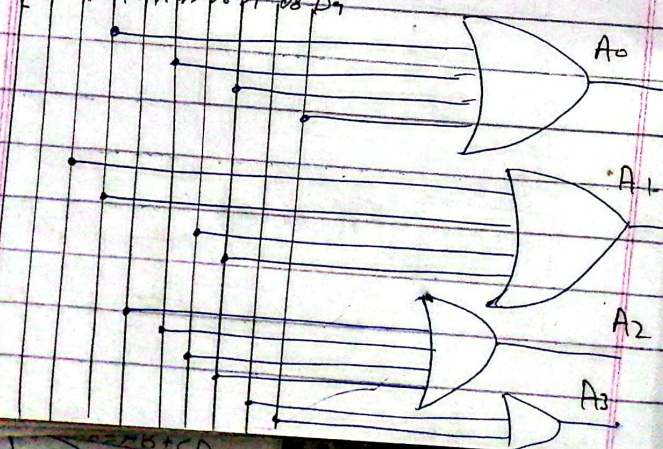

Code Converter:-

BCD-to-Binary Conversion:-

One method of BCD-to-binary code conversion uses adder circuits.

The basic conversion is:

→ The binary numbers representing the weights of the BCD bits are summed to produce the total binary number.

BCD Bit	BCD weight	Binary Representation						
		(MSB)	64	32	16	8	4	(LSB)
A ₀	1	0	0	0	0	0	0	1
A ₁	2	0	0	0	0	0	1	0
A ₂	4	0	0	0	0	1	0	0
A ₃	8	0	0	0	1	0	0	0
B ₀	10	0	0	0	1	0	1	0
B ₁	20	0	0	1	0	1	0	0
B ₂	40	0	1	0	1	0	0	0
B ₃	80	1	0	1	0	0	0	0

Code Conversion:-

BCD-to-Binary Conversion:-

One method of BCD-to-binary code conversion uses adder circuits.

The basic conversion is:


→ The binary numbers representing the weights of the BCD bits are summed to produce the total binary number.

BCD Bit	BCD weight	Binary Representation							
		(MSB)	64	32	16	8	4	2	(LSB)
A ₀	1		0	0	0	0	0	0	1
A ₁	2		0	0	0	0	0	1	0
A ₂	4		0	0	0	0	1	0	0
A ₃	8		0	0	0	1	0	0	0
B ₀	10		0	0	0	1	0	1	0
B ₁	20		0	0	1	0	1	0	0
B ₂	40		0	1	0	1	0	0	0
B ₃	80		1	0	1	0	0	0	0


Convert the binary numbers
0101 to Gray code with
ex-OR gates.

Solution:

$(0101)_2 \xrightarrow{GC} 0111$

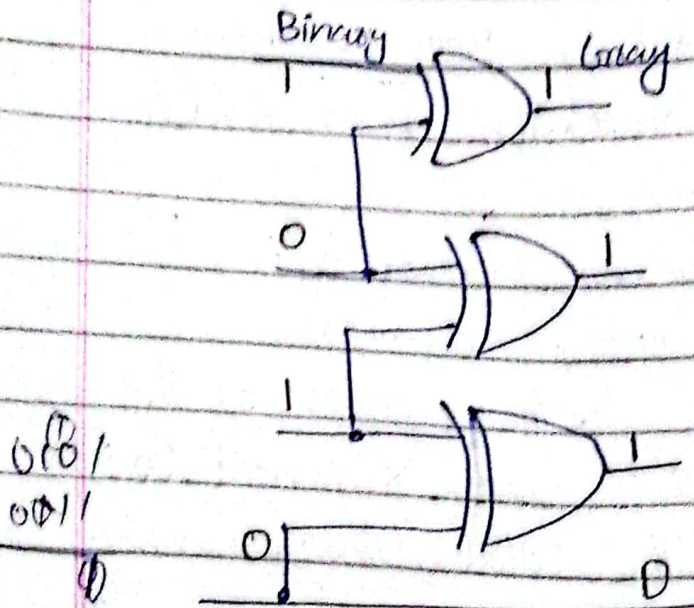

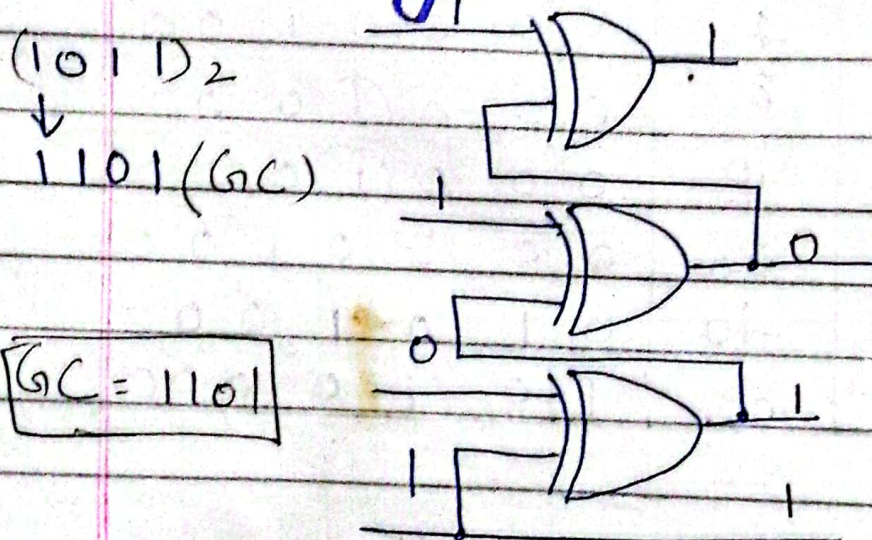0111
Convert the Gray code
1011 To binary with
ex-OR gates



$GC = 1101$

Date _____

Q# What is difference b/w encoder and decoder?

Encoder

→ Encoder circuit basically converts the applied information signal into a coded digital bit stream.


→ It has 2^n input.

→ The output lines are n .

→ The encoder circuit is installed at the transmitting end.

→ OR gate is the basic logic element used in it.

Logic diagram:

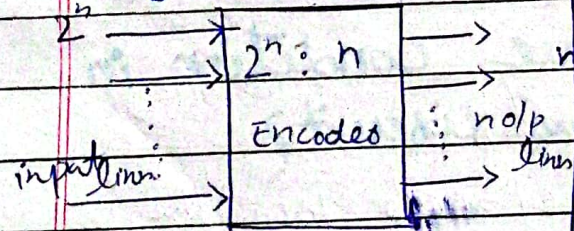

e.g:

Calculator, voice mail, video encoders

Decoder


→ Decoder performs the reverse operation and recovers the original information from the coded bits.

→ It has n inputs.

→ The output lines are 2^n .

→ The decoder circuit is installed at the receiving side.

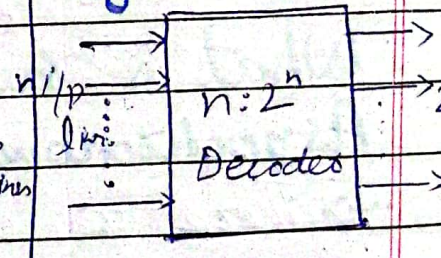→ AND gate along with Not gate is the basic element in logic diagram:-



e.g:

microprocessors, memory chips etc.